

ECE 6473

Lecture 2

Date: 09/21/2015

Shaloo Rakheja

Assistant Professor

Electrical and Computer Engineering, NYU

# Reading


- Power point and hand-written lecture notes posted on [newclasses.nyu.edu](http://newclasses.nyu.edu)
- Sections 3.3.1–3.3.2, 5.1—5.4 from Digital Integrated Circuits by Jan M. Rabaey et al.

# MOSFET analysis


- Recap from 09/14/2015
  - MOSFET I-V characteristics
  - Transistor Resistance
  - *Sub-threshold Conduction (read from posted lecture notes and discuss in office hours)*
- MOSFET capacitance
- Introduction to Inverter functionality

# MOSFET

n-MOSFET

 

p-MOSFET

 

CMOS process has two types of transistors: NFET and PFET

# MOSFET

	NFET	PFET
Body or substrate	p-doped	n-doped
Source/Drain contacts	n+ doped	p+ doped
Current	Flows from drain to source ( $I_{DS}$ )	Flows from source to drain ( $I_{SD}$ )
Current carriers	Electrons	Holes
Threshold voltage	Positive	Negative
Relevant terminal voltages	$V_{gs}, V_{ds}, V_{bs}$	$V_{sg}, V_{sd}, V_{sb}$

- In MOSFETs, threshold voltage is the control voltage. It tells whether or not the transistor is conducting.
- Threshold voltage is fixed by the fabrication process.

# NFET I-V characteristics

## Modes of operation

$$V_{gs} < V_{Tn}$$

Cut-off or “OFF”

**Ideally in cut-off, the transistor must not conduct any current.**

$$V_{gs} \geq V_{Tn}$$

Active or “ON”

Linear

$$V_{ds} < V_{gs} - V_{Tn}$$


Saturation

$$V_{ds} \geq V_{gs} - V_{Tn}$$

**$(V_{gs} - V_{Tn})$  is the SATURATION voltage**

# NFET I-V model for hand calculation

Active region:  $V_{gs} \geq V_{Tn}$

 

Linear ( $V_{ds} < V_{gs} - V_{Tn}$ ): 
$$I_{DS} = (\mu_n C_{ox}) \left( \frac{W}{L} \right) \left[ (V_{gs} - V_{Tn}) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

Saturation ( $V_{ds} \geq V_{gs} - V_{Tn}$ ): 
$$I_{DS} = \frac{1}{2} (\mu_n C_{ox}) \left( \frac{W}{L} \right) (V_{gs} - V_{Tn})^2 (1 + \lambda V_{ds})$$

$\kappa_n = (\mu_n C_{ox})$ : Process parameter  $\rightarrow$  decided by the foundry.

Designers CANNOT tweak it.

$\beta_n = \kappa_n \times (W/L) \rightarrow$  Designers can tweak  $W/L$  ratio. Hence,  $\beta_n$  is a design parameter.

$\lambda$ : Channel-length modulation. Also considered fixed by foundry.

# Threshold voltage, $V_{Tn}$

$$V_{Tn} = V_{T0} + \gamma \left( \sqrt{(2|\phi_f| - V_{bs})} - \sqrt{2|\phi_f|} \right)$$

$V_{T0}$ : Process parameter. Fixed by the foundry.


$\gamma$ : Body-effect coefficient. Fixed by the foundry.

$\phi_f$ : Bulk Fermi potential. Fixed by the foundry

- $V_{Tn}$  is fixed by the foundry.
- Designers can control  $V_{bs}$  voltage through circuit design.
- When  $V_{bs} = 0V$ ,  $V_{Tn}$  cannot be tweaked.




# NFET I-V characteristics

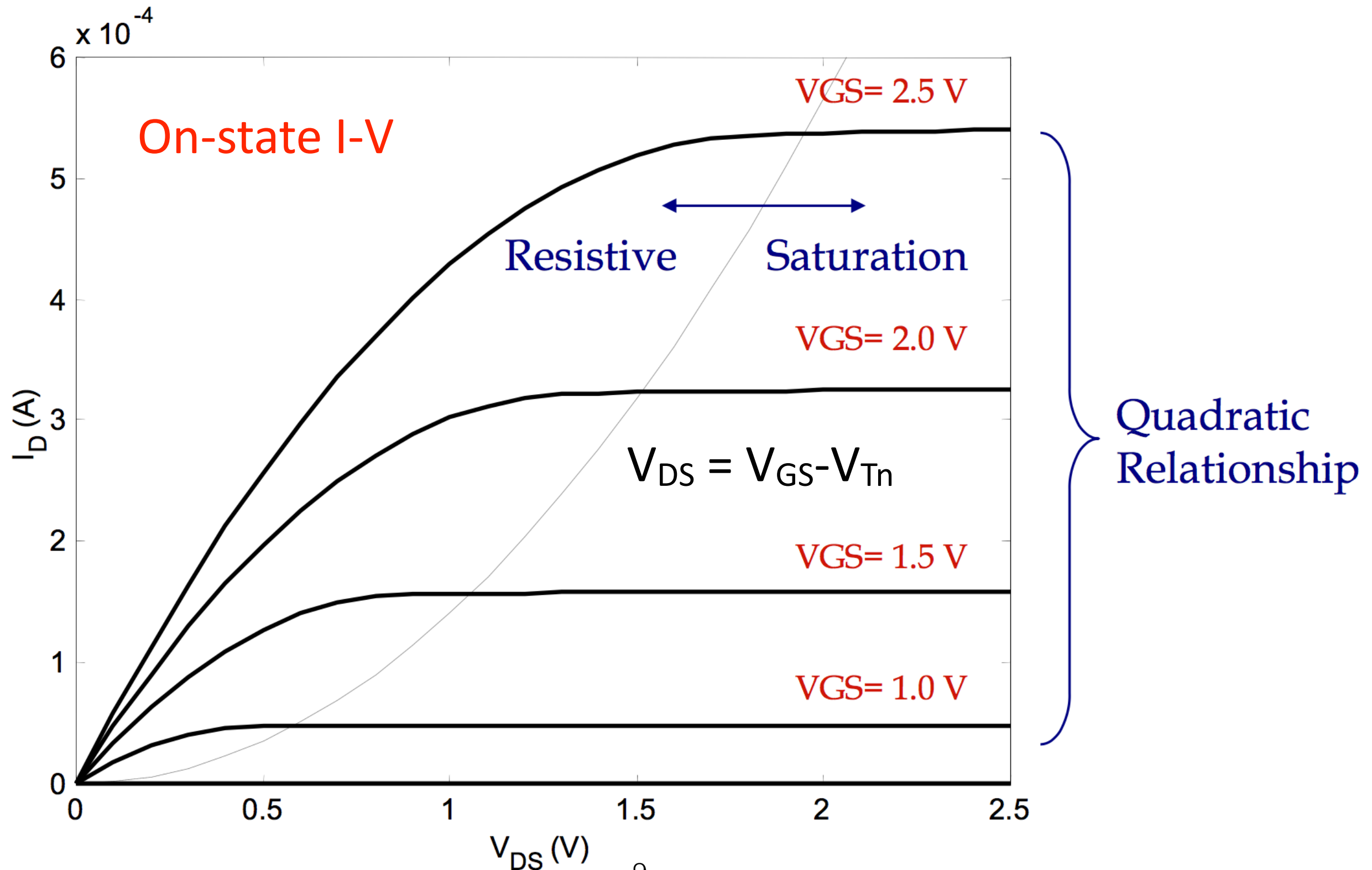

# PFET I-V model for hand calculation

Active region:  $V_{sg} \geq |V_{Tp}|$

 

Linear ( $V_{sd} < V_{sg} + V_{Tp}$ ): 
$$I_{SD} = (\mu_h C_{ox}) \left( \frac{W}{L} \right) \left[ (V_{sg} + V_{TP}) V_{sd} - \frac{V_{sd}^2}{2} \right]$$

Saturation ( $V_{sd} \geq V_{sg} + V_{Tp}$ ): 
$$I_{SD} = \frac{1}{2} (\mu_h C_{ox}) \left( \frac{W}{L} \right) (V_{sg} + V_{TP})^2 (1 + \lambda V_{sd})$$

$\kappa_p = (\mu_h C_{ox})$ : Process parameter  $\rightarrow$  decided by the foundry.


Designers CANNOT tweak it.

$\beta_p = \kappa_p \times (W/L) \rightarrow$  Designers can tweak  $W/L$  ratio. Hence,  $\beta_p$  is a design parameter.


$\lambda$ : Channel-length modulation. Also considered fixed by foundry.
 
# NFET versus PFET

In CMOS digital design, we will use both NFETs and PFETs for complementary logic.



$$\beta_n = \kappa_n \times (W/L)_n$$

 

$$\beta_p = \kappa_p \times (W/L)_p$$

Very important point: For the same  $C_{ox}$ ,  $\kappa_n > \kappa_p$

# Differential resistance of the transistor

**Differential resistance** of the transistor is a useful concept for analog design. It is also called small signal resistance.

$$r = \left( \frac{\partial I_{DS}}{\partial V_{ds}} \right)^{-1}$$

Linear region

$$r = \frac{1}{\mu_n C_{ox} \left( \frac{W}{L} \right) \left[ (V_{gs} - V_{Tn}) - V_{ds} \right]}$$

Saturation region

$$r = \frac{2}{\mu_n C_{ox} \left( \frac{W}{L} \right) (V_{gs} - V_{Tn})^2 \lambda}$$

If  $\lambda = 0$ , then  $r = \infty$  (ideal current source).

Very useful for designing current mirror circuits in analog space.

# Large signal resistance of the transistor

Large signal resistance of the transistor is a useful concept for digital design.

$$R = \left( \frac{\Delta I_{DS}}{\Delta V_{ds}} \right)^{-1}$$

Say  $V_{gs} = V_{dd}$

$V_{ds}$  changes from 0 to  $V_{dd}$

What is  $R$ ?

When  $V_{ds} = 0V$ ,  $I_{DS} = 0$ .

When  $V_{ds} = V_{dd}$ ,  $I_{DS} = \text{Saturation current}$

# Large signal resistance of the transistor

Large signal resistance of the transistor is a useful concept for digital design.

$$R = \left( \frac{\Delta I_{DS}}{\Delta V_{ds}} \right)^{-1}$$

Say  $V_{gs} = V_{dd}$

$V_{ds}$  changes from 0 to  $V_{dd}$

When  $V_{ds} = 0V$ ,  $I_{DS} = 0$ .

When  $V_{ds} = V_{dd}$ ,  $I_{DS} = \text{Saturation current}$

What is  $R$ ?


$$R = \left( \frac{I_{DS,sat}}{V_{dd}} \right)^{-1}$$

*Substitute  $I_{DS,sat}$  in this equation*


$$\frac{2V_{dd}}{(\mu_n C_{ox}) \left( \frac{W}{L} \right) (V_{dd} - V_{Tn})^2 (1 + \lambda V_{dd})}$$

# Problem:
 
## Discharging time of a capacitor through a NFET



 Question:  
Obtain the time constant for discharging of the capacitor through the NFET.



$$\tau = 0.69 R_{eq} C$$


$$R_{eq} = \frac{1}{2} (R_1 + R_2)$$

Large signal resistance  
at  $V_{ds} = V_{dd}$

Large signal resistance  
at  $V_{ds} = V_{dd}/2$

# Problem:
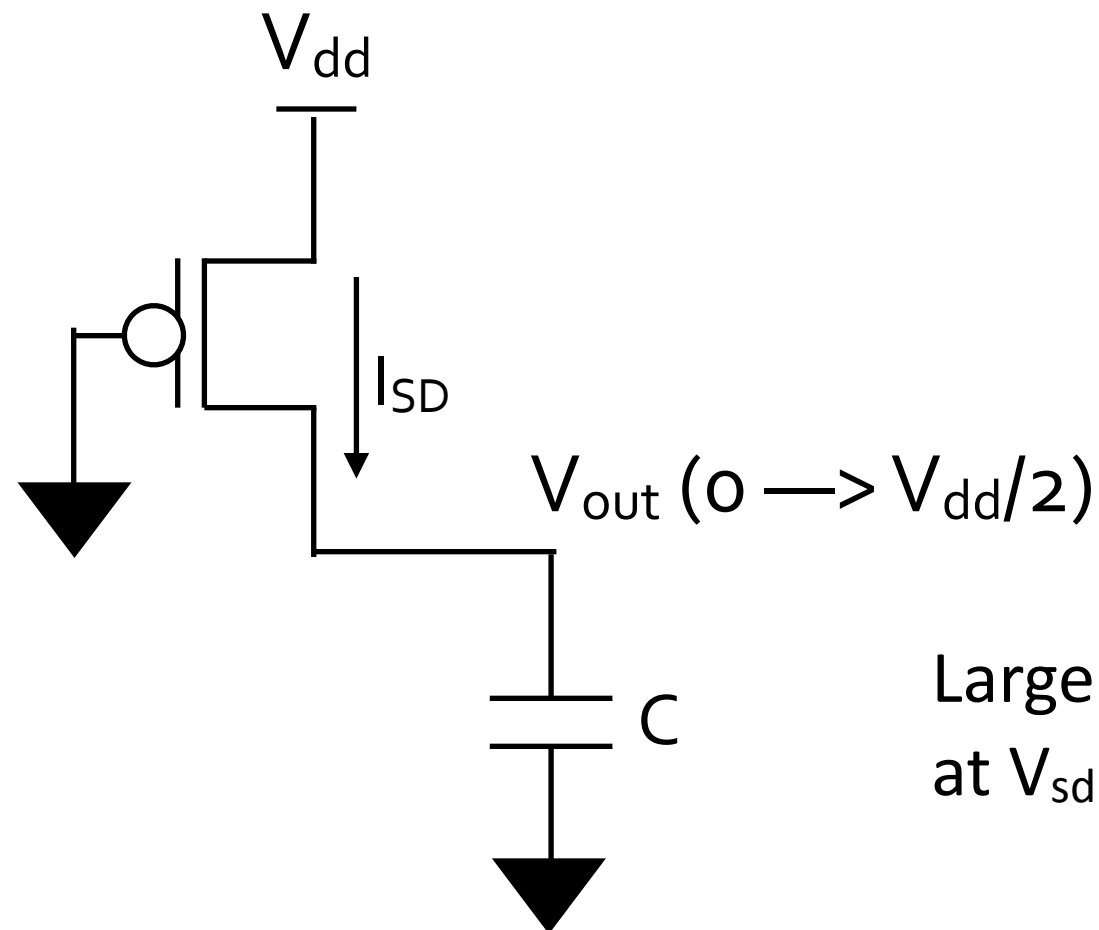
## Charging time of a capacitor through a PFET



$$\tau = 0.69 R_{eq} C$$



$$R_{eq} = \frac{1}{2} (R_1 + R_2)$$

Large signal resistance  
at  $V_{sd} = V_{dd}$

Large signal resistance  
at  $V_{sd} = V_{dd}/2$


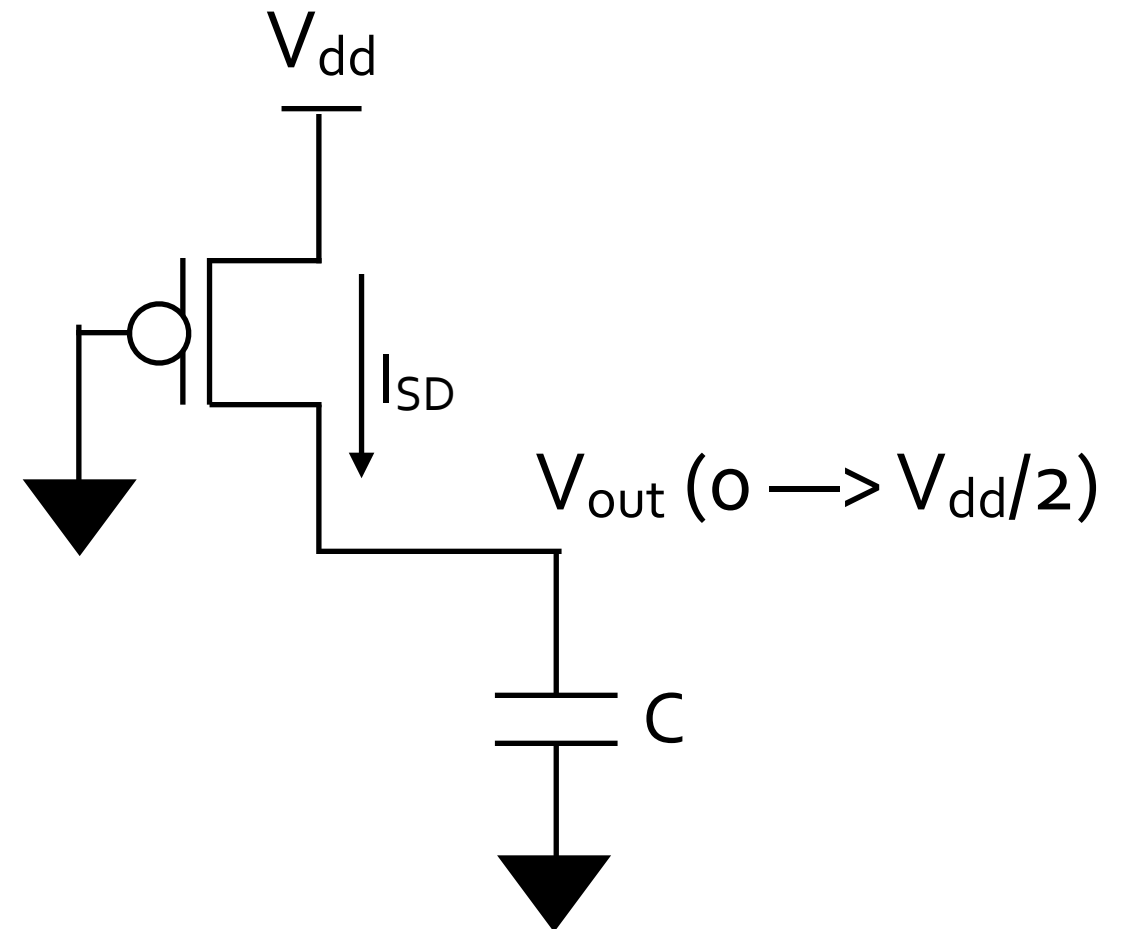 
# Calculating equivalent resistance, $R_{eq}$



$$R_{eq} = \frac{3V_{dd}}{4I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{dd} \right)$$

$$I_{DSAT} = \frac{1}{2} (\mu C_{ox}) \left( \frac{W}{L} \right) [(V_{dd} - V_T)^2]$$

Use the values of  $\mu$ ,  $C_{ox}$ ,  $V_T$ ,  $(W/L)$  corresponding to either NFET or PFET depending on analysis.

# Equivalent resistance


$$R_{eq} = \frac{3V_{dd}}{2(\mu C_{ox})\left(\frac{W}{L}\right)(V_{dd} - V_T)^2} \left(1 - \frac{5}{6}\lambda V_{dd}\right)$$

Observations:

$(W/L) \uparrow$ ,  $R_{eq} \downarrow$

$(\mu C_{ox}) \uparrow$ ,  $R_{eq} \downarrow$

$V_{dd} \downarrow$ ,  $R_{eq} \uparrow$

 

*Try the MATLAB file given in class*

# Equivalent resistance in Jan. M. Rabaey's book

The analysis we have presented in class is based on averaging the resistances to find  $R_{eq}$ .

**A more accurate analysis is given in Eq. (3.41) and (3.42) in Chapter 3 of Jan M. Rabaey's book.**

Using the approach in the book, the value of  $R_{eq}$  is given as

$$R_{eq} = \frac{3V_{dd}}{4I_{DSAT}} \left( 1 - \frac{7}{9} \lambda V_{dd} \right)$$
$$I_{DSAT} = \frac{1}{2} (\mu C_{ox}) \left( \frac{W}{L} \right) [(V_{dd} - V_T)^2]$$


→ This factor changes.  
Not a big deal, since  
mostly  $\lambda V_{dd} \ll 1$ .

## Summary: charging and discharging of capacitors through NFET and PFET

- Time constant of charging and discharging of capacitance is always given as  $\tau = 0.69 R_{eq} C$
- $R_{eq}$ : Equivalent resistance of the transistor.
- To compute  $R_{eq}$ , we must take average of initial resistance of transistor ( $R_1$ ) and value at half way through the transition ( $R_2$ ).
- That is,  $R_{eq} = \frac{1}{2} (R_1 + R_2)$
- C is the total capacitance that is being charged or discharged.
 
# Summary: charging and discharging of capacitors through NFET and PFET

Time constant of charging and discharging of capacitance is always given as  $\tau = 0.69 R_{eq} C$




## Summary: charging and discharging of capacitors through NFET and PFET

- If NFET is used to discharge the capacitor, the final voltage across the capacitor will be 0.
- If PFET is used to charge the capacitor, the final voltage across the capacitor will be  $V_{dd}$ .


In CMOS logic:

- when a circuit “node” needs to be discharged to ground, we must use NFET to discharge. NFETs form the **pull-down network (PDN)** in CMOS logic.
- When a circuit “node” needs to be charged to  $V_{dd}$ , we must use PFET to charge. PFETs form the **pull-up network (PUN)** in CMOS logic.

# The MOSFET capacitance

 

# The MOSFET capacitance

 

- a. Gate capacitance
- b. Source overlap capacitance
- c. Drain overlap capacitance
- d. Source-body junction capacitance
- e. Drain-body junction capacitance

all capacitances depend on width and length of the device.


Except for gate capacitance, other capacitances are parasitic capacitances.



# The MOSFET capacitance

- The gate capacitance is the gate voltage dependent capacitance of the Metal-Oxide-Semiconductor structure and depends on the oxide material and the oxide thickness.
- The overlap caps are between gate and source/drain terminals. They are parasitic caps. and does not contribute to the charge. The importance of the overlap cap will be introduced later in “Miller effect” discussion.
- The junction capacitances are due to p-n junction between the n+ source/drain and p-type body (for NFET). They are also parasitic capacitances and depends on the junction doping and drain-to-body and source-to-body biases.
- All capacitances depends on the length and/or width of the devices.

# The gate and overlap capacitance

 



*gate capacitance:*

$$C_{gate} = C_{ox}WL = \frac{\epsilon}{t_{ox}}WL$$

*overlap capacitance:*


$$C_{ov} = C_{ox}WX_{ov} = \frac{\epsilon}{t_{ox}}WX_{ov}$$

# The gate capacitance

  

For digital logic we are most interested in “on” (i.e. inversion) and “off” (i.e. in accumulation or weak depletion) devices.

# Junction or Diffusion capacitance

 


$$C_{Junction} = C_{bottom} + C_{sidewall} = C_j \times AREA + C_{jsw} \times PERIMETER$$

$$= C_j W L_s + C_{jsw} (W + 2L_s)$$

$C_j$  &  $C_{jsw}$  are technology and voltage dependent parameter

# Junction or Diffusion capacitance

 

Highly non-linear  
(voltage-dependent)

$$C_j = \frac{C_{j0}}{\left(1 - \frac{V_{jun}}{\phi_0}\right)^m}$$


$C_{j0}$ : junction capacitance under zero bias

$V_{jun}$ : junction voltage (negative for reverse biased junctions)

$\phi_0$ : built-in junction bias

$m$ : grading coefficient (1/3 (linear junction) or 1/2 (abrupt jn.))

# Junction or Diffusion capacitance

 

$$C_j = \frac{C_{j0}}{(1 - V_D / \phi_0)^m}$$

$m = 0.5$ : abrupt junction  
 $m = 0.33$ : linear junction

# Linearizing junction capacitance

An easy way to linearize the junction capacitance is given as

$$C_j = k_{eq} C_{j0}$$
$$k_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1-m)} \left[ (\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m} \right]$$

- The factor  $k_{eq}$  is the linearizing factor.
- $C_{j0}$  is the junction capacitance per unit area under zero bias conditions.

# Model for manual analysis

*gate capacitance:*

$$C_{gate} = \frac{\epsilon}{t_{ox}} WL$$


*overlap capacitance:*

$$C_{ov} = \frac{\epsilon}{t_{ox}} W X_{ov}$$

*Junction capacitance:*

$$C_{Junction} = C_j WL_S + C_{jsw} (W + 2L_S)$$

$C_j$  &  $C_{jsw}$  are tech. param.

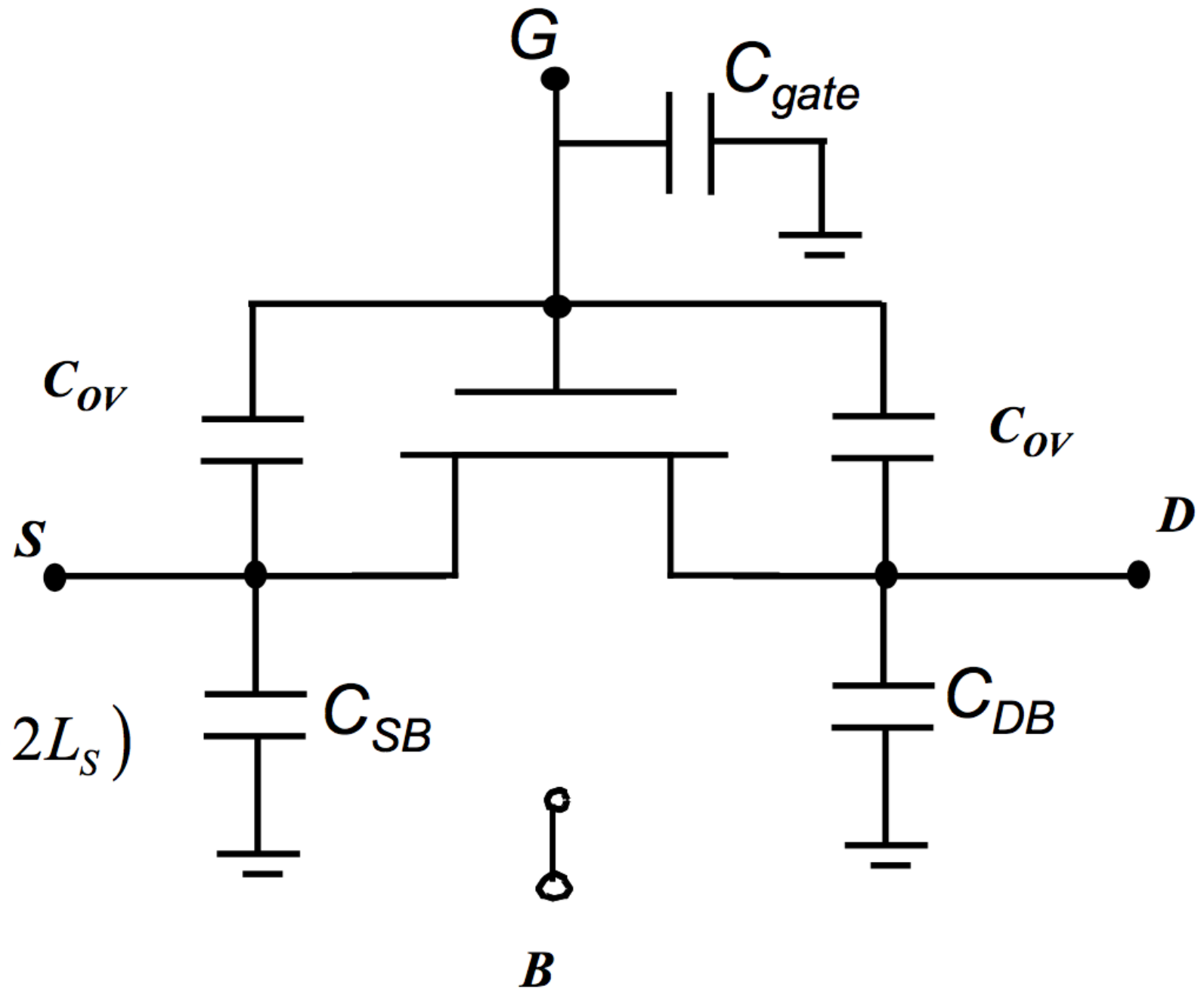






## CMOS inverter analysis

- a. Steady state or DC operation
- b. Switching characteristics
- c. Power dissipation

# CMOS inverter


- Rail-to-rail voltage swing
- Logic levels are independent of device sizes – ratioless logic
- Low-impedance path to  $V_{dd}$  or ground
- Infinite input impedance – infinite drivability
- No direct path between  $V_{dd}$  and ground in steady state

# CMOS inverter

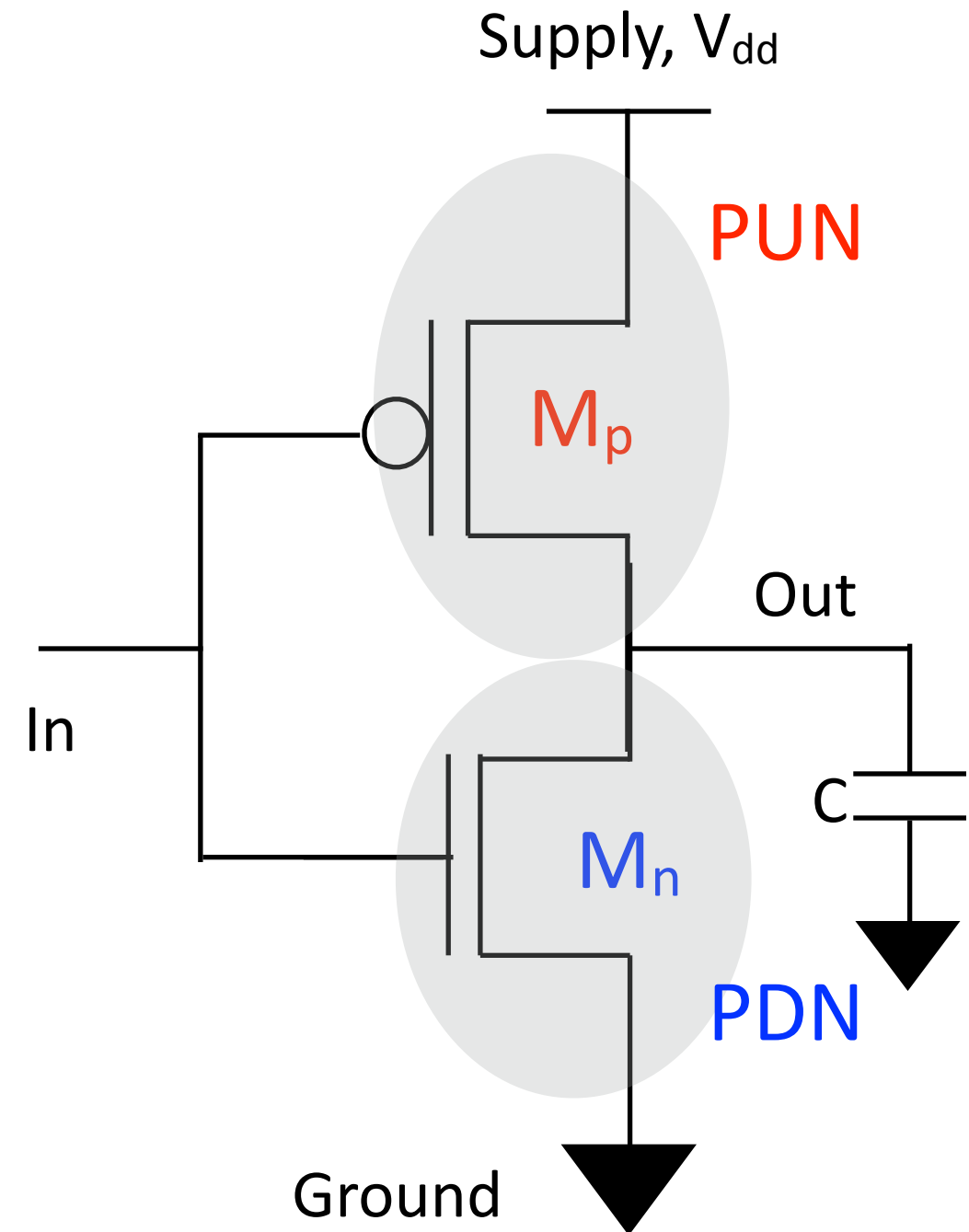  

- The PFET ( $M_p$ ) is good at pulling up "C" to  $V_{dd}$ .
- The NFET ( $M_n$ ) is good at pulling down "C" to ground.

# Inverter functionality

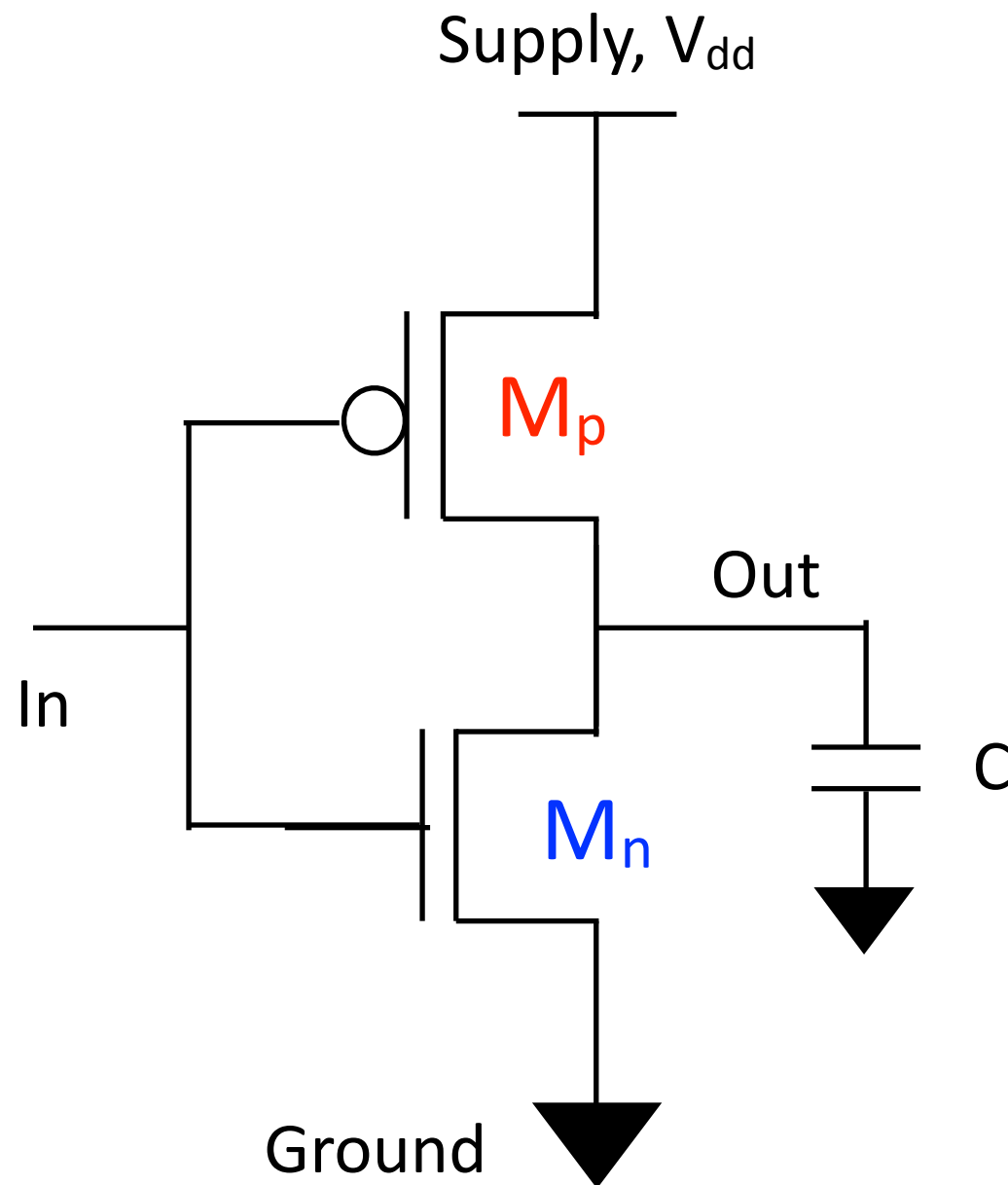

$$\beta_p = \kappa_p \times (W/L)_p$$


$$\beta_n = \kappa_n \times (W/L)_n$$

Typically:  $\kappa_n > \kappa_p$

Why:


Because  $\mu_n > \mu_h$

# Inverter functionality

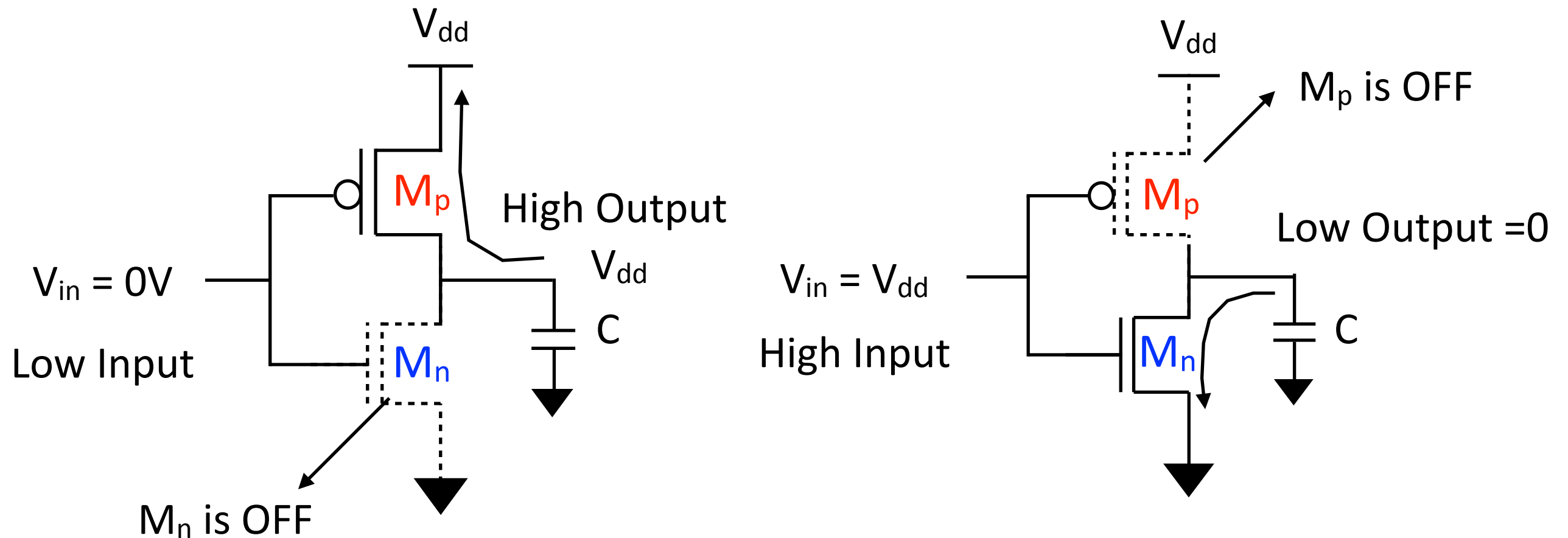

Low output level = 0  
High output level =  $V_{dd}$
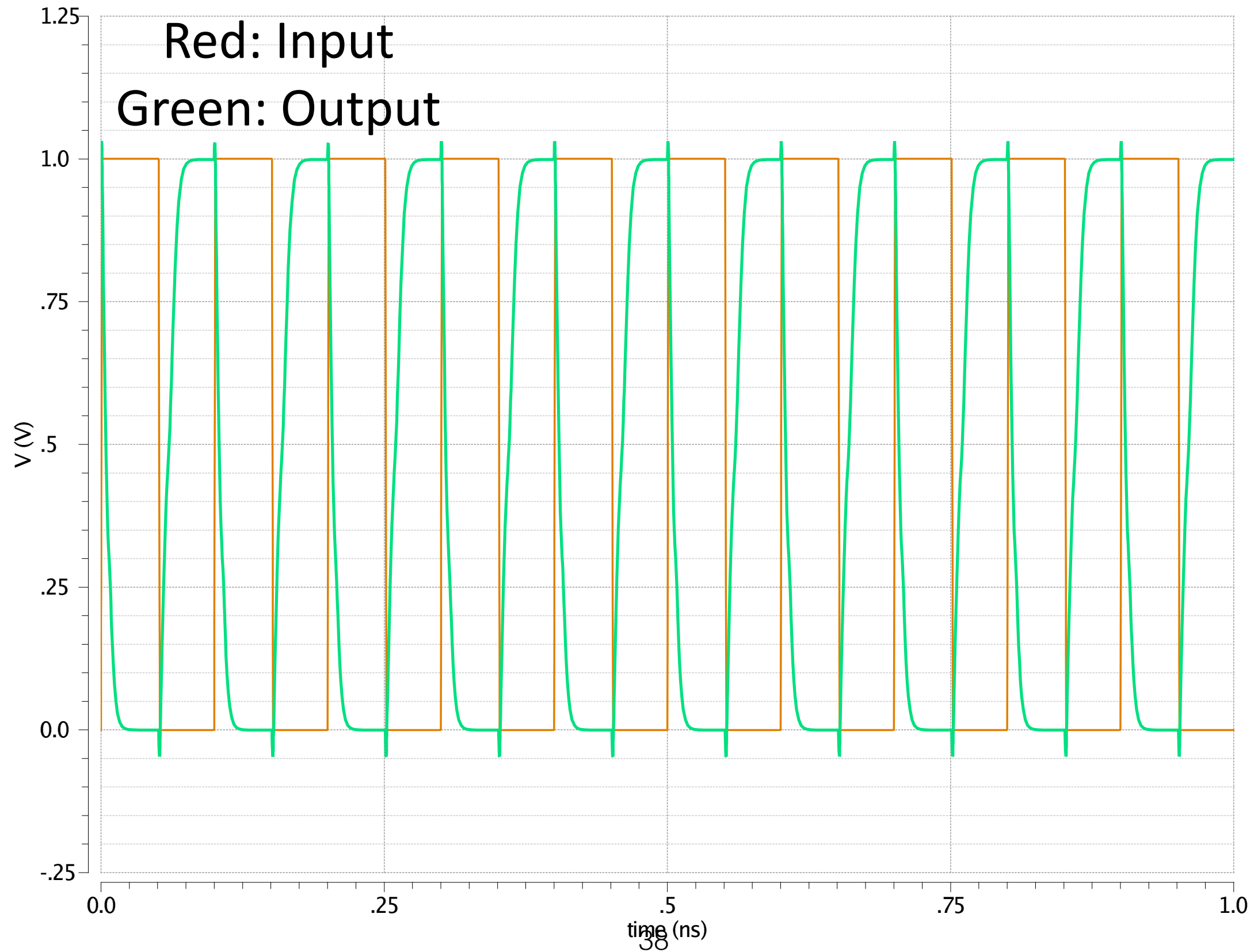
# Inverter transient response (HSPICE sim.)




# CMOS inverter analysis

Steady state or DC characteristics

*Robustness and noise tolerance*

 
# Voltage transfer characteristics (VTC)

VTC tells us  $V_{out}$  versus  $V_{in}$  for the inverter.





# Voltage transfer characteristics (VTC)

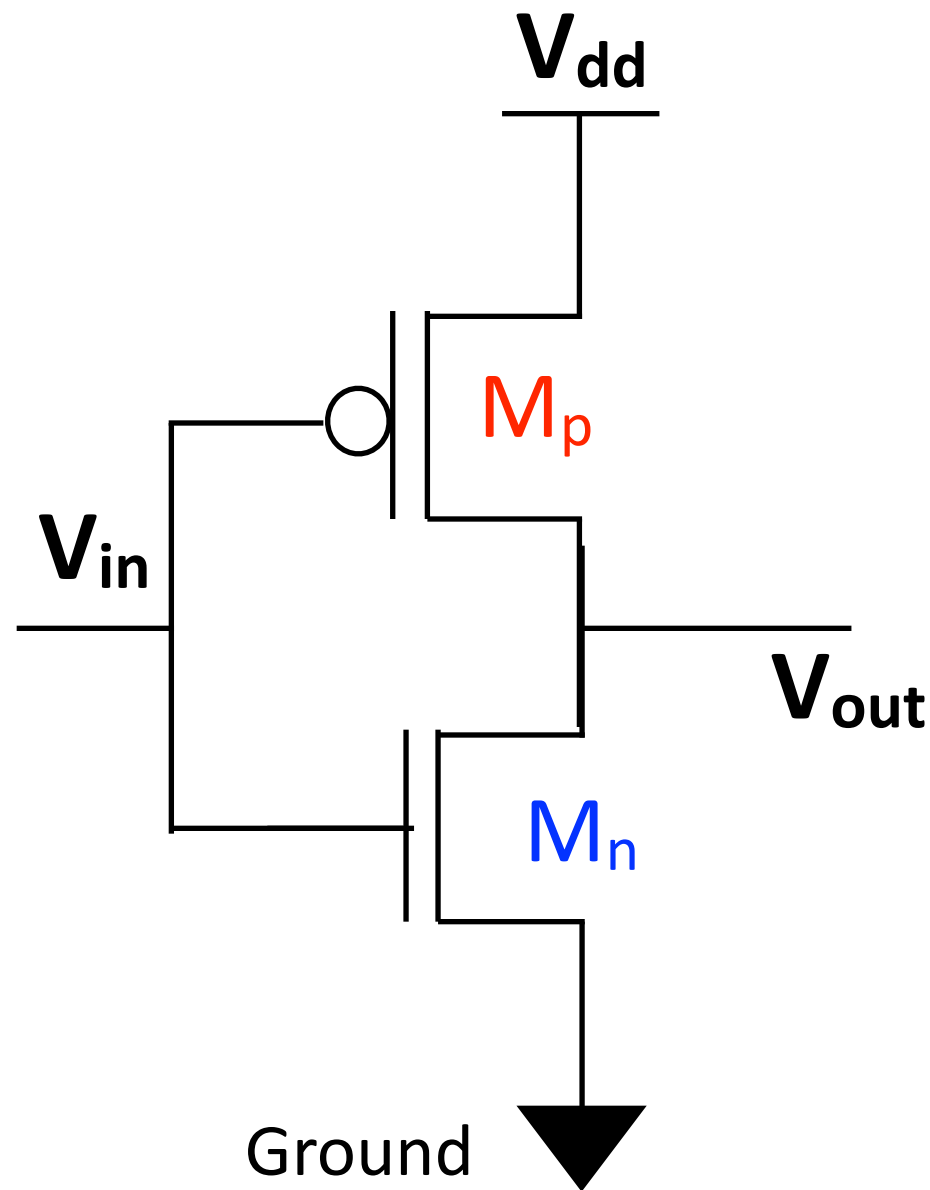

VTC tells us  $V_{out}$  versus  $V_{in}$  for the inverter.

*Voltage conditions:*

**NFET:**  $V_{gsn} = V_{in}$ ,  $V_{dsn} = V_{out}$

**PFET:**  $V_{sgp} = V_{dd} - V_{in}$ ,  $V_{sdp} = V_{dd} - V_{out}$

*DC characteristics:*

$$I_{NFET}(V_{gsn}, V_{dsn}, V_{thn}) = I_{PFET}(V_{sgp}, V_{sdp}, V_{thp})$$

**Key: Need to determine the operating region of NFET and PFET for different input and output voltage**

# Voltage transfer characteristics (VTC)

*DC characteristics:*

$$I_{NFET}(V_{gsn}, V_{dsn}, V_{thn}) = I_{PFET}(V_{sgp}, V_{sdp}, V_{thp})$$

*NFET Regions*

*cut – off* :  $V_{in} < V_{thn}, V_{out} \sim V_{DD}$  :

*saturation* :  $V_{in} > V_{thn}, V_{out} > V_{in} - V_{thn}$

*linear* :  $V_{in} > V_{thn}, V_{out} < V_{in} - V_{thn}$


*PFET Regions*

*linear* :  $V_{in} < V_{DD} - |V_{thp}|, V_{DD} - V_{out} < V_{DD} - V_{in} - |V_{thp}|$


*saturation* :  $V_{in} < V_{DD} - |V_{thp}|, V_{DD} - V_{out} > V_{DD} - V_{in} - |V_{thp}|$

*cut – off* :  $V_{in} > V_{DD} - |V_{thp}|, V_{out} \sim 0$
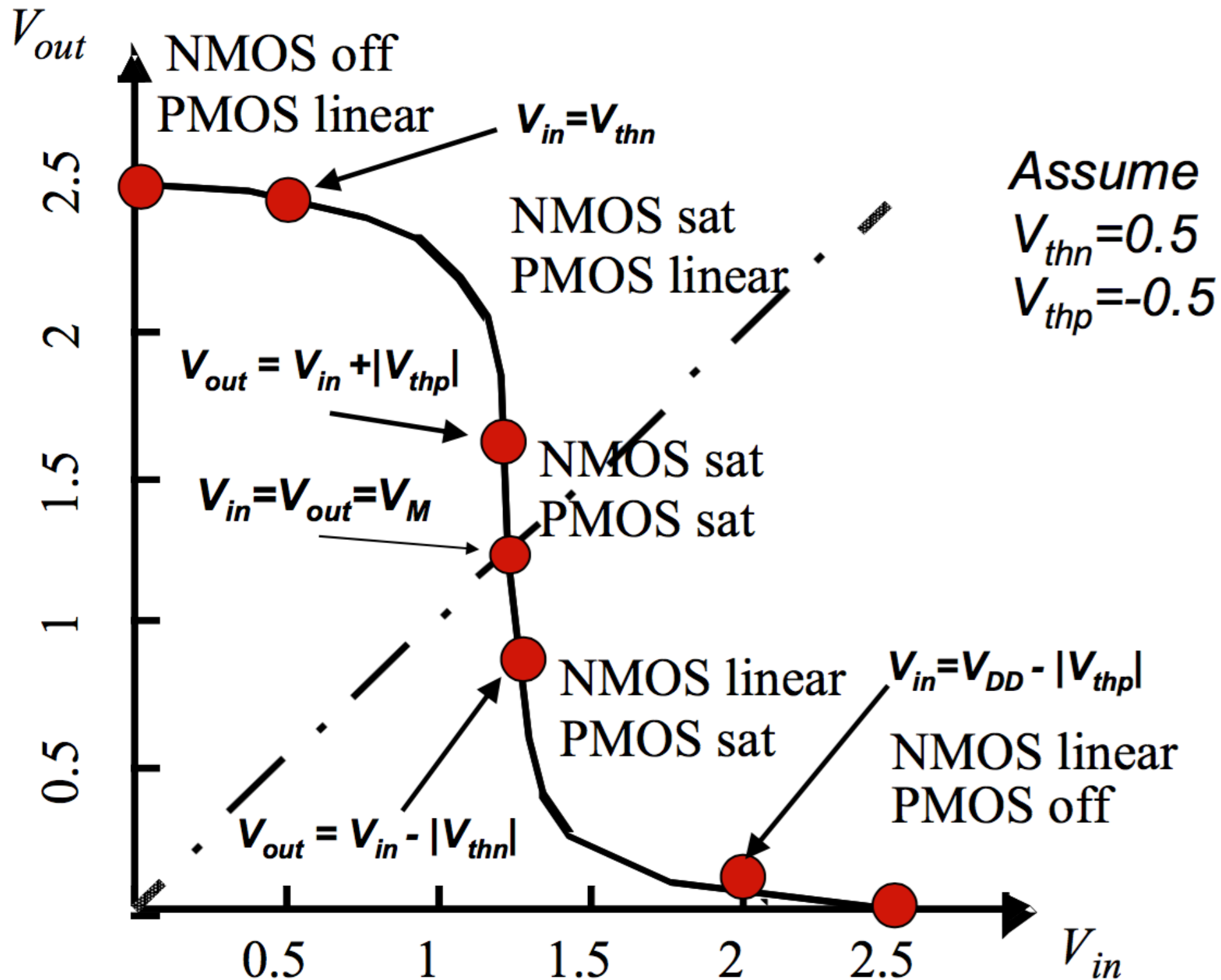
# Voltage transfer characteristics (VTC) graphically explained




# Switching threshold voltage

 

$V_M = V_{out} = V_{in} \rightarrow$  known as switching threshold or the trip point.

# Noise margins


 


**“a” and “b” are points with gain = 1**

**$V_{IL}$ : low noise margin**

**$V_{IH}$ : high noise margin**
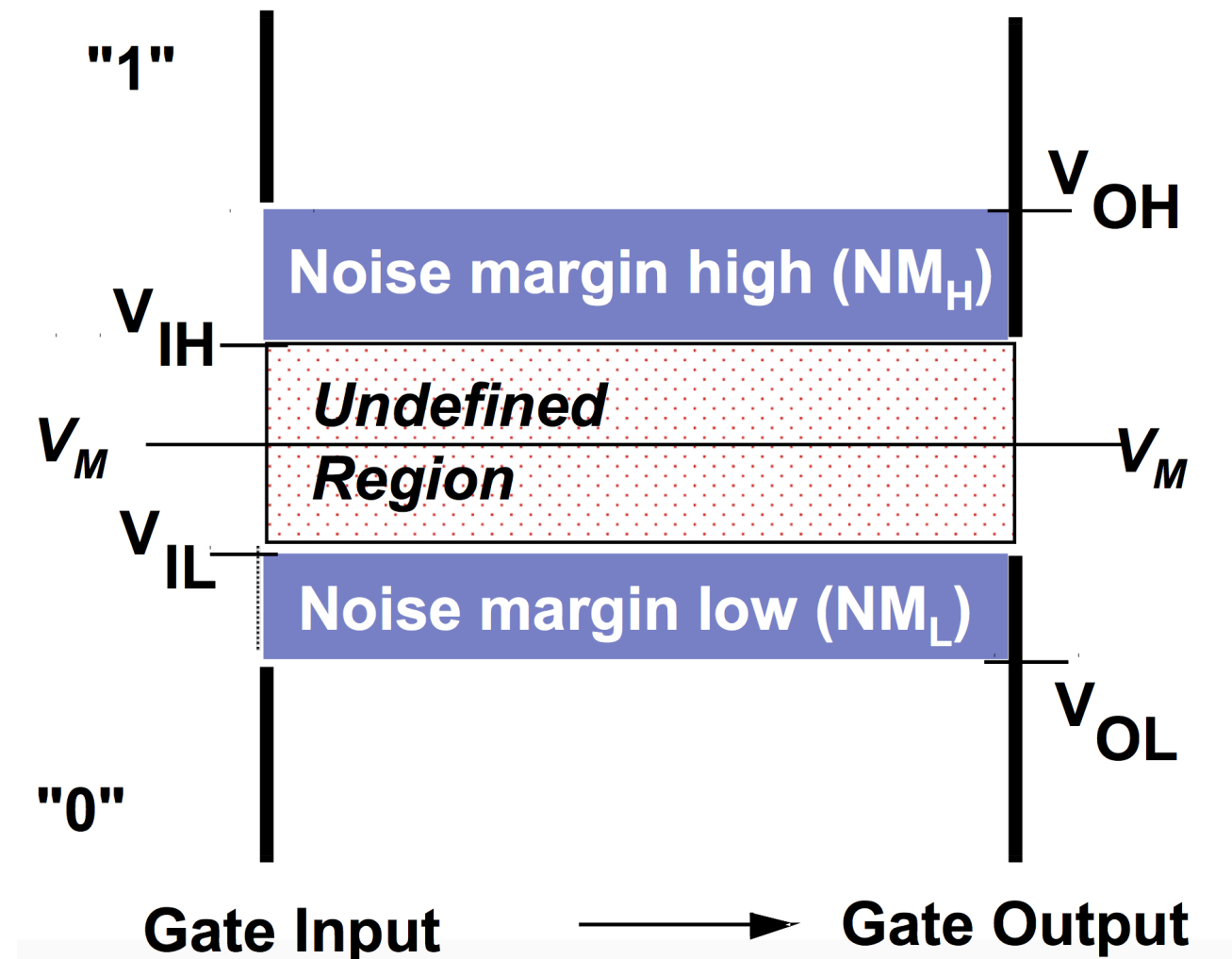 
# What do noise margins signify physically?



- Noise margins signify robustness to noise.
- An input signal within  $(0, V_{IL})$  voltage levels will always be considered as logic "0" or LOW.
- An input signal within  $(V_{IH}, V_{DD})$  levels will always be considered as logic "1" or HIGH.

# Switching threshold ( $V_M$ ) computation

**At  $V_{in} = V_{out} = V_M$ , both NFET and PFET are saturated.**

$$V_M = \frac{V_{dd} - |V_{Tp}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{Tn}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

Recall:



$$\beta_n = (\mu_n C_{ox})(W/L)_n$$
$$\beta_p = (\mu_p C_{ox})(W/L)_p$$

$$\text{For } V_M = rV_{DD} \Rightarrow \sqrt{\frac{\beta_n}{\beta_p}} = \frac{(1-r)V_{DD} - |V_{thp}|}{(rV_{DD} - V_{thn})}$$

To achieve  $V_M = 0.5V_{DD}$  with  $|V_{thp}| = V_{thn} \Rightarrow \beta_n / \beta_p = 1$

Normally,  $\mu_n / \mu_p = 2$ ,  $W_p / L_p = 2(W_n / L_n)$  (assuming,  $C_{oxp} = C_{oxn}$ )

# Design of switching threshold

  

Stronger PFET  $\rightarrow$  difficult high-to-low transition  $\rightarrow$  higher switching threshold ( $V_M$ )

Stronger NFET  $\rightarrow$  difficult low-to-high transition  $\rightarrow$  low switching threshold ( $V_M$ )

Proper choice of  $(\beta_n/\beta_p)$  is necessary to achieve a desired switching threshold ( $V_M$ )




# CMOS inverter analysis


Switching characteristics

*Performance (speed)*
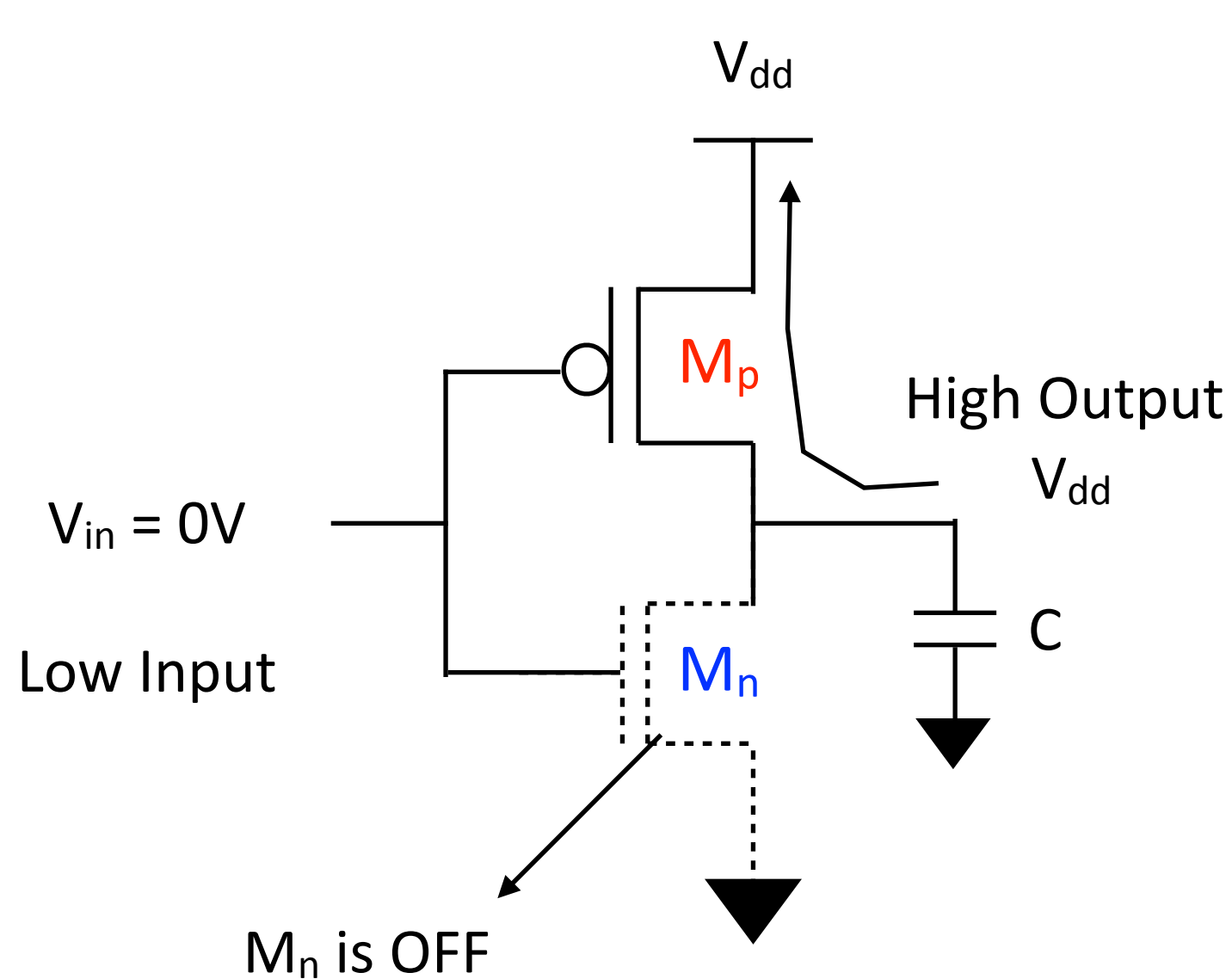
# Low to high transition time in inverter




 Input: High  $\rightarrow$  Low  
Output: Low  $\rightarrow$  High




$$t_{pLH} = 0.69 R_{eq,p} C$$
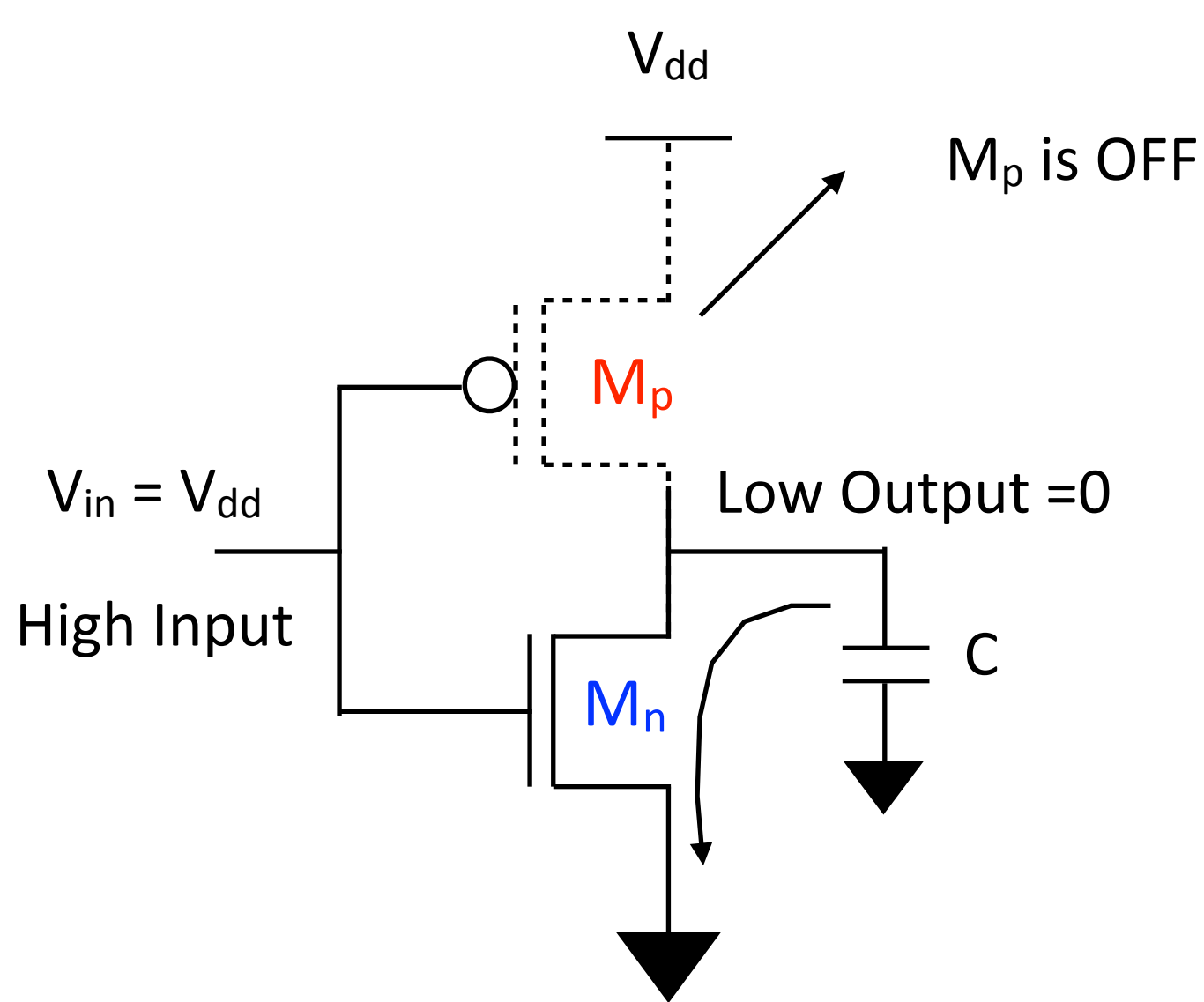
# High to low transition time in inverter




 Input: Low  $\rightarrow$  High  
Output: High  $\rightarrow$  Low




$$t_{pHL} = 0.69 R_{eq,n} C$$

# Inverter transient response

 
 
# Inverter transient response from HSPICE



Propagation delay

$$t_p = 0.5(t_{pLH} + t_{pHL})$$

$$= 0.69C_L \frac{(R_{eq,n} + R_{eq,p})}{2}$$

**Rise time:**

10% to 90% of  $V_{dd}$

$$t_r = \ln(9)R_{eq,p}C_L$$

**Fall time:**

90% to 10% of  $V_{dd}$

$$t_f = \ln(9)R_{eq,n}C_L$$

# Inverter transient response from HSPICE

## Propagation delay

$$t_p = 0.5(t_{pLH} + t_{pHL})$$
$$= 0.69C_L \frac{(R_{eq,n} + R_{eq,p})}{2}$$

## **Rise time:**

10% to 90% of  $V_{dd}$

$$t_r = \ln(9)R_{eq,p}C_L$$

## **Fall time:**

90% to 10% of  $V_{dd}$

$$t_f = \ln(9)R_{eq,n}C_L$$

Next class we will study more details of inverter sizing based on desired fall time, rise time ...

# Next class on 09/28/2015

- Recap from 09/21/2015
  - MOSFET capacitances
  - Inverter DC characteristics
  - Definitions of rise time, fall time, propagation delay
- Calculation of inverter delay and sizing
- Power dissipation of inverter