HW-2

Chi Zhang

09/27/2015

$\mathbf{Q}\mathbf{1}$

a

As $V_{GS} = V_{DD} - V_{OH}$ and only when $V_{OH} \leq V_{DD} - V_{Th}$ could guarentee the transistor is turned on. And the maximum value is the output voltage before t = 0

$$V_{OH} = V_{DD} - V_{Th}$$

$$= V_{DD} - V_{T0} - \gamma(\sqrt{2|\phi_F| + V_{OH}} - \sqrt{2|\phi_F|})$$

$$- (1)$$

 \mathbf{c}

When $t \to \infty$,

$$V_{out} = I_{DSAT}R_{SW}$$

$$= \frac{(V_{DD} - V_{out})R_{SW}}{\frac{1}{2}\kappa[V_{DD} - V_{out} - V_{T0} - \gamma(\sqrt{2|\phi_F|} + V_{out} - \sqrt{2|\phi_F|})]^2}$$

$$= (2)$$

b

As informed in the question, V_{Th} is constant and is the average of its maximum and minimum, which is

$$V_{Th} = V_{T0} + \frac{1}{2}\gamma(\sqrt{2|\phi_F| + V_{OH}} + \sqrt{2|\phi_F| + V_{out}}) - \gamma\sqrt{2|\phi_F|}$$
= (3)

As $V_{out} = V_{OH} \rightarrow V_{OH}/2$, $V_{DS} = V_{DD} - V_{OH} \rightarrow V_{DD} - V_{OH}/2$. Thus,

$$R_{eq} = \frac{1}{2} \left[\frac{V_{DD} - V_{OH}}{\frac{1}{2} \kappa (V_{DD} - V_{OH} - V_{Th})^2} + \frac{V_{DD} - V_{OH}/2}{\frac{1}{2} \kappa (V_{DD} - V_{OH}/2 - V_{Th})^2} \right]$$

$$= \frac{V_{DD} - V_{OH}}{\kappa (V_{DD} - V_{OH} - V_{Th})^2} + \frac{V_{DD} - V_{OH}/2}{\kappa (V_{DD} - V_{OH}/2 - V_{Th})^2}$$
(4)

 $\mathbf{Q2}$

$$V_X = V_{DD} - I_{SD}R_1$$

$$= V_{DD} + \frac{1}{2}\kappa \frac{W}{L}(V_X - V_{in} + V_{Th})^2 [1 + \lambda(V_X - V_{in})]R_1$$

$$=$$
(5)

 \mathbf{a}

b

$$1.5(V) = 2.5(V) - 0.5 \times (-30)^{-6} (A/V^2) \times \frac{W}{L} \times (1.5(V) - 0.4(V))^2 \times (1 - 0.1(V^{-1}) \times a.5(V)) \times 20 \times 10^3(\Omega)$$
(6)

Thus,

$$\frac{W}{L} = 3.24\tag{7}$$

 $\mathbf{Q3}$

 \mathbf{a}

$$t_{tLH} = 0.69 R_{eq} C_L$$

$$-$$
(8)

b

$$\Delta t_{pLH} = 0.69 R_{eq} C_0 W_0$$

$$=$$

$$(9)$$

 \mathbf{c}

$$t_{pHL} = 0.69RC_L$$

$$= (10)$$

 \mathbf{d}