 


ECE 6473 HW-3 solution

Problem 1.

a) $F = \overline{(A+B)CD}$

b)



c) High-to-Low Delay:

Initial: $A = 1, B = 0, C = 1, D = 0$ (or $A=0, B=1, C = 1, D = 0$)

Final: $A = 1, B = 0, C = 1$, and $D = 1$ (or $A = 0, B = 1, C = 1$, and $D = 1$)

$A = 1$ (or $B = 1$), $C = 1$ will charge all the intermediate node capacitance and D makes a transition from 0 to 1.

Low-to-High Delay:

Initial: $A = 0, B = 1, C = 1, D = 1$

Final: $A = 0, B = 0, C = 1, D = 1$

B makes a 1 to 0 transition. This transition needs to charge the intermediate node capacitance in the series path (i.e. A and B) from V_{tp} to V_{DD} and the output from 0 to V_{DD} .

Problem 2.

(a) To derive energy in one complete cycle for the chain of inverters:

$$E_{total} = \sum_{j=1,N} E_j$$

Where E_j is the energy of the j^{th} stage.

$$E_j = V_{DD}^2 \cdot C_1 u^j$$

$$E_{total} = \sum_{j=1 \dots N} C_1 V_{DD}^2 u^j = C_1 V_{DD}^2 \cdot u \cdot \frac{u^N - 1}{u - 1}$$

$$E_{total} = C_1 V_{DD}^2 \cdot \frac{u}{u - 1} \cdot \left(\frac{C_L}{C_1} - 1 \right)$$

$$E_{total}(\text{in terms of } E_r) = E_r \cdot \frac{u}{u - 1} \cdot \left(\frac{C_L}{C_1} - 1 \right)$$

(b) To derive the expression for EDP in terms of reference EDP and to find the expression that optimized EDP

Using the fact that the delay of the chain is: $Nu\tau_r$

$$EDP_{chain} = E_r \cdot \frac{u}{u - 1} \cdot \left(\frac{C_L}{C_1} - 1 \right) \cdot Nu\tau_r$$

Using the fact that $N = \ln\left(\frac{C_L}{C_1}\right) / \ln(u)$

$$EDP_{chain} = E_r \tau_r \cdot \frac{u^2}{u-1} \cdot \left(\frac{C_L}{C_1} - 1 \right) \cdot \frac{\ln\left(\frac{C_L}{C_1}\right)}{\ln(u)}$$

$$\frac{EDP_{chain}}{EDP_{ref}} = \ln\left(\frac{C_L}{C_1}\right) \cdot \left(\frac{C_L}{C_1} - 1 \right) \cdot \left[\frac{u^2}{\ln(u) \cdot (u-1)} \right]$$

To optimize the EDP:


$$\frac{\partial}{\partial u} \left(\frac{EDP_{chain}}{EDP_{ref}} \right) = 0$$

$$u^2 \ln(u) - 2u \ln(u) - u(u-1) = 0$$

$$\ln(u) (u-2) - (u-1) = 0$$

$$\ln(u) = \frac{u-1}{u-2}$$

 
$$\mathbf{u_{opt} = e^{\frac{u_{opt}-1}{u_{opt}-2}}}$$



From Fig. 2, the optimum value of sizing is obtained as ~ 4.2443

The optimal value of “u” for delay optimization is equal to $e = 2.72$ (for FET capacitance = 0).
The optimized value of “u” for EDP is more than that for delay optimization.

Problem 3:

 

First, we calculate path effort.

$$g1 = (1+2r) / (1+r) = 6/3.5 = 1.71$$

$$g2 = (2+r) / (1/r) = 4.5/3.5 = 1.29$$

$$g3 = g1 = 1.71$$

$$G = g1 * g2 * g3 = 3.772$$

$$H = 10C / C = 10$$

$$B = C_{total} / C_{path} = (2+r+3+r) / (2+r) = 10/4.5 = 2.22$$

$$F = G H B = 83.8$$

$$f = F^{1/3} = 4.38$$

We now work backwards.

$$h3 = 10C * (6/3.5) / 4.38 = 3.91 C$$

$$h2 = 3.91C * (4.5/3.5) / 4.38 = 1.15 C$$

$$h1 = 2.22 * 1.15C * (6/3.5) / 4.38 = C$$