

HW-2

Chi Zhang

09/27/2015

Q1

a

As $V_{GS} = V_{DD} - V_{OH}$ and only when $V_{OH} \leq V_{DD} - V_{Th}$ could guarantee the transistor is turned on. And the maximum value is the output voltage before $t = 0$.

$$\begin{aligned} V_{OH} &= V_{DD} - V_{Th} \\ &= V_{DD} - V_{T0} - \gamma(\sqrt{2|\phi_F| + V_{OH}} - \sqrt{2|\phi_F|}) \end{aligned} \quad (1)$$

Therefore,

$$2|\phi_F| + V_{OH} + \gamma(\sqrt{2|\phi_F| + V_{OH}}) - (V_{DD} - V_{T0} + \sqrt{2|\phi_F|} + 2|\phi_F|) = 0 \quad (2)$$

So,

$$\sqrt{2|\phi_F| + V_{OH}} = -\frac{\gamma}{2} + \sqrt{\frac{\gamma^2}{4} + V_{DD} - V_{T0} + \gamma\sqrt{2|\phi_F|} + 2|\phi_F|} \quad (3)$$

Then, finally:

$$\begin{aligned} V_{OH} &= \frac{\gamma^2}{2} + V_{DD} - V_{T0} + \gamma\sqrt{2|\phi_F|} \\ &\quad - \gamma\sqrt{\frac{\gamma^2}{4} + V_{DD} - V_{T0} + \gamma\sqrt{2|\phi_F|} + 2|\phi_F|} \\ &= V_{DD} - 0.4 \times \sqrt{V_{DD} + 0.52} - 0.04(V) \end{aligned} \quad (4)$$

c

When $t \rightarrow \infty$,

$$\begin{aligned} V_{out} &= I_{DSAT}R_{SW} \\ &= \frac{1}{2}\kappa[V_{DD} - V_{out} - V_{T0} - \gamma(\sqrt{2|\phi_F| + V_{out}} - \sqrt{2|\phi_F|})]^2 R_{SW} \\ &= \end{aligned} \quad (5)$$

b

As informed in the question, V_{Th} is constant and is the average of its maximum and minimum, which is

$$V_{Th} = V_{T0} + \frac{1}{2}\gamma(\sqrt{2|\phi_F| + V_{OH}} + \sqrt{2|\phi_F| + V_{OH}/2}) - \gamma\sqrt{2|\phi_F|} \quad (6)$$

$$=$$

As $V_{out} = V_{OH} \rightarrow V_{OH}/2$, $V_{DS} = V_{DD} - V_{OH} \rightarrow V_{DD} - V_{OH}/2$. Thus,

$$R_{eq} = \frac{1}{2} \left[\frac{V_{DD} - V_{OH}}{\frac{1}{2}\kappa(V_{DD} - V_{OH} - V_{Th})^2} + \frac{V_{DD} - V_{OH}/2}{\frac{1}{2}\kappa(V_{DD} - V_{OH}/2 - V_{Th})^2} \right] \quad (7)$$

$$= \frac{V_{DD} - V_{OH}}{\kappa(V_{DD} - V_{OH} - V_{Th})^2} + \frac{V_{DD} - V_{OH}/2}{\kappa(V_{DD} - V_{OH}/2 - V_{Th})^2}$$

$$=$$

Q2

$$V_X = V_{DD} - I_{SD}R_1$$

$$= V_{DD} + \frac{1}{2}\kappa\frac{W}{L}(V_X - V_{in} + V_{T0})^2(1 + \lambda V_X)R_1 \quad (8)$$

$$=$$

a

b

$$\frac{W}{L} = 3.24 \quad (9)$$

Q3

a

$$t_{tLH} = 0.69R_{eq}C_L \quad (10)$$

$$=$$

b

$$\Delta t_{pLH} = 0.69R_{eq}C_0W_0 \quad (11)$$

$$= t_0$$

c

$$t_{pHL} = 0.69RC_L \quad (12)$$

$$=$$

d

With $\beta_n = \beta_p$, and $|\gamma_n| = |\gamma_p|$ with $|\lambda_n| = |\lambda_p|$ from the table coming with questions. $\frac{t_{pLH,n}}{t_{pLH,p}}$ becomes,

$$\begin{aligned} \frac{t_{pLH,n}}{t_{pLH,p}} &= \frac{R_{eq,n}}{R_{eq,p}} \\ &= \frac{1 - \lambda_n(V_{DD} - V_{out})}{1 - |\lambda_p|(V_{DD} - V_{out})} \end{aligned} \quad (13)$$

With situation mentioned above, $R_{eq,n} > R_{eq,p}$, thus it will be slower usein PFET.

Q4