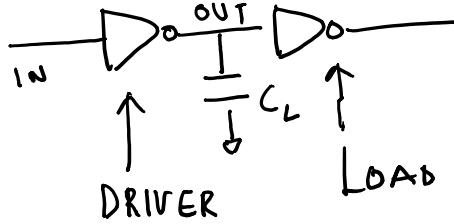


Optimal choice of NFET/PFET ratio (slides 38-40)

Saturday, September 26, 2015 8:44 PM



ASSUME :- Load size = Driver size

That is, $(W/L)_{LOAD} = (W/L)_{DRIVER}$ for both PFET/NFET.

Lets say $(W_p/W_n) = \alpha$ for both LOAD & DRIVER.

Ques:- What should ' α ' be for minimum delay?

$$C_L = (1 + \alpha) \underbrace{C_{FET-n}}_{\text{Parasitic}} + C_w + (1 + \alpha) \underline{C_{gn}} \rightarrow \text{gate capacitance}$$

$$t_d = 0.5 \frac{C_L V_{DD}}{(V_{DD} - V_T)^2} \left(\frac{1}{\beta_n} + \frac{1}{\beta_p} \right) \quad V_{TN} = |V_{TP}| = V_T$$


$$\text{For } C_L = (1 + \alpha) C_{FET-n} + C_w + (1 + \alpha) C_{gn}$$

We see that t_d is a non-monotonic function of ' α '.

∴ For minimum delay, one must solve

$$\frac{\partial t_d}{\partial \alpha} = 0 \Rightarrow \boxed{\alpha_{opt} = \sqrt{\frac{\mu_n}{\mu_p}} \sqrt{1 + \frac{C_w}{C_{FETn} + C_{gn}}}}$$

Final Answer

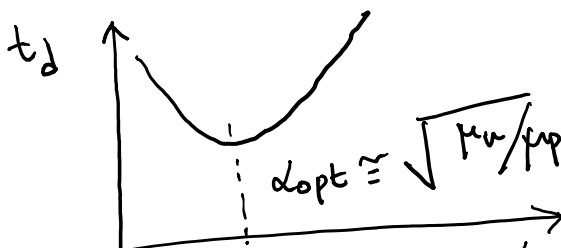

$$\mu_n > \mu_p$$

$$\text{Typically } \mu_n = 2 \mu_p$$

α

$= 1.414$

For $\frac{\mu_n}{\mu} \approx 2.0$

Typically $\mu_n = 2\mu$
So $\alpha_{opt} \approx 1.414$