 


# Sizing inverters for performance

Saturday, September 26, 2015 11:12 PM

By sizing we mean adjusting the widths of PFET and NFET to achieve a given set of design constraints.



$L_p = L_n = \text{minimum set by the technology}$

Let's say  $\frac{W_p}{W_n} = \alpha$  where  $W_n = W_{\text{unit}}$

Let's say we choose ' $\alpha$ ' such that  $R_p = R_n = R_{\text{unit}}$ .


With this we can achieve  $t_{pLH} = t_{pHL}$  if  $V_{tn} = |V_{tp}| = V_t$

$$t_d = 0.69 R_{\text{unit}} C_L$$

The input capacitance of this inverter will be  $C_{in} = (1 + \alpha) C_{gn}$  since  $C_{gp} = \alpha C_{gn}$

Remember:- gate capacitance scales with the width.

## 2 inverter chain

 

At this time, we ignore the device parasitic capacitances

$$t_d = t_{d,inv1} + t_{d,inv2}$$

$$t_{d,inv1} = 0.69 R_{\text{unit}} (u C_{in})$$

$$t_{d,inv2} = 0.69 \frac{R_{\text{unit}}}{u} (C_L)$$

$$t_d = 0.69 R_{\text{unit}} C_{in} \left[ u + \underbrace{\frac{C_L}{C_{in}}}_f \cdot \frac{1}{u} \right]$$

$f$  = Fan-out

$t_{po}$

$f$


Fan-out tells us the ratio of the net load capacitance to the input gate capacitance of the first inverter.

$$t_d = t_{po} [u + f/u] \quad \text{where } t_{po} = 0.69 R_{unit} C_{in}$$

to minimize  $t_d \Rightarrow \frac{\partial t_d}{\partial u} = 0 \Rightarrow u_{opt}$

$$\boxed{u_{opt} = \sqrt{f}} \\ t_{d,opt} = 2 \sqrt{f} t_{po}$$

 Sizing a chain of inverters for driving a large load



$$C_2 = u C_1 \\ C_3 = u C_2 = u^2 C_1 \\ C_N = u^N C_1$$

Each inverter is sized " $u$ " times bigger than the previous stage.

$$t_{d,j} = 0.69 R_j C_{j+1} = 0.69 \frac{R_{unit}}{u^j} (u^{j+1} C_1) \\ = \underbrace{0.69 R_{unit} C_1 u}_{\tau_r \text{ or } t_{po}}$$

$$t_{d,j} = \tau_r u$$

$$t_d = \sum_{j=1}^N \tau_r u = N u \tau_r$$

What is  $N$ ?  $\frac{C_L}{C_1} = u^N$  so  $N = \frac{\ln(\overbrace{C_L/C_1}^{\text{Fan-out}})}{\ln(u)} = \frac{\ln(f)}{\ln(u)}$


$$t_d = \frac{\ln(f)}{\ln(u)} u \tau_r$$

$\dots \dots \dots t_d \Rightarrow \frac{\partial t_d}{\partial u} = 0 \Rightarrow u_{opt}$

$$\text{Minimize } t_d \Rightarrow \frac{\partial t_d}{\partial u} = 0 \Rightarrow u_{opt}$$

$$\boxed{\begin{matrix} u_{opt} = 2 \\ N_{opt} = \ln(f) \end{matrix}} \Rightarrow \text{No parasitics were considered.}$$

 Sizing a chain of inverters with parasitics



Each capacitance now comes from the input cap. of the following stage and the parasitic cap. of that particular stage.

$$t_{d,j} = 0.69 R_j \left[ \underbrace{C_{FET,j}}_{\text{Parasitic}} + \underbrace{C_{g,j+1}}_{\text{gate}} \right]$$

$$t_{d,j} = 0.69 \frac{R_{unit}}{u^j} \left[ C_{FET,1} u^j + C_1 u^{j+1} \right]$$

$$t_{d,j} = 0.69 R_{unit} C_{FET,1} + 0.69 R_{unit} C_1 u$$

$$t_d = \sum_{j=1}^N t_{d,j} = \underbrace{0.69 R_{unit} C_{FET,1} N}_{\tau_x \text{ "PARASITIC"}} + \underbrace{0.69 R_{unit} C_1 N u}_{\tau_r}$$

$$t_d = \underbrace{\tau_x N}_{\text{Does not depend on}} + \tau_r N u$$

Does not depend on  $u$ .

does not  
depend on  
the sizing at all.

$$N = \frac{\ln(f)}{\ln(u)}$$

minimize  $t_d \Rightarrow \frac{\partial t_d}{\partial u} = 0 \Rightarrow u_{opt}$

$$u_{opt} [\ln(u_{opt}) - 1] = \tau_x / \tau_r = \frac{C_{FET,1}}{C_1}$$

$$N_{opt} = \frac{\ln(f)}{\ln(u_{opt})}$$

$$f = C_L / C_1$$

↓  
FAN-OUT

FINAL  
RESULT

Note:- When  $\frac{\tau_x}{\tau_r} \ll 1$

then  $u_{opt} = e$

Also, when  $\tau_x$  is non-negligible, then # stages needed to optimize the delay are fewer than would be the case without  $\tau_x$ .