 


**ECE 6473**  
**Homework # 3**  
**Date Assigned: October 9<sup>th</sup>, 2015**  
**Due Date: October 19<sup>th</sup>, 2015 @ 11.59 PM**

**Grading:**  
**Problem 1: 30 points**  
**Problem 2: 40 points**  
**Problem 3: 30 points**


Problem 1: Consider the following circuit



- a. What is the logic function implemented by the CMOS transistor network?
- b. Size the NMOS and PMOS devices so that the output resistance is the same as that of an inverter with an NMOS  $W/L = 1$  and PMOS  $W/L = 2$ .
- c. Consider a step input and only **one input is allowed to make a transition** at one time. What are the input patterns that give the worst case  $t_{pHL}$  and  $t_{pLH}$ . State clearly what are the initial input patterns and what are the final patterns (mention which input has to make a transition) in order to achieve this maximum propagation delay. Consider the effect of the capacitances at the internal nodes.

## Problem 2: Sizing Optimization for Delay, Energy, and Energy-Delay product

Consider the following inverter chain.

 

Assume, the reference delay as:  $\tau_r = 0.69R_1C_1$  and reference energy as:  $E_r = C_1V_{DD}^2$  where,  $R_1$  is the resistance of the first stage (the ratio  $\alpha$  is chosen such that PMOS and NMOS have same resistance). The reference energy delay product is  $EDP_{ref} = E_r\tau_r$ . Neglect  $C_{FET}$  in the entire analysis.

- Derive an expression for the total energy dissipated in the chain for one complete swing of the input (i.e. low-to-high + high-to-low) (assume  $u > 1$ ) in terms of ' $u$ ',  $E_r$ ,  $C_L$ , and  $C_1$ .
- Derive the expression for normalized Energy-Delay Product ( $EDP_{chain}/EDP_{ref}$ ) of the chain in terms of ' $u$ ',  $E_r$ ,  $C_L$ , and  $C_1$ . Find out the relation that provides the optimal ' $u$ ' for minimum normalized EDP.
- Now consider  $C_L = 256C_1$ . First, find out the optimal ' $u$ ' that provides minimum normalized EDP. You can vary ' $u$ ' from 2 to 10 in very fine steps ( $< 0.001$ ) and find out when the optimal relation obtained from (b) is satisfied. How does it differ from the optimal ' $u$ ' for minimum delay for same  $C_L$ ?

**Problem 3: Find  $C_1/C$  and  $C_2/C$  that results in optimal delay.**

The logic chain in the following figure is constructed with  $r = 2.5$ . Determine the optimum input capacitance (with respect to  $C$ ) for each stage to achieve a minimum delay through the 'red' colored path using the Logical Effort method. Assume the NAND3 gate in the branch point is a unit-size NAND3 gate i.e. its pull-up and pull-down resistances are same as that of a reference inverter.

