

HW-4

Chi Zhang

14/10/2015

Problem 1

Problem 2

Problem 3

a

t_{pLH} for C_a should equals to t_{pLH} for C_L , hence,

$$\begin{aligned} R_n C_a \ln\left(\frac{1}{1 - \frac{\Delta V_a}{V_{DD} - V_{Tn}}}\right) &= R_n C_L \ln\left(\frac{1}{1 - \frac{\Delta V_{out}}{V_{DD}}}\right) \\ \frac{C_a}{C_L} &= \frac{\ln\left(\frac{1}{1 - \frac{\Delta V_{out}}{V_{DD}}}\right)}{\ln\left(\frac{1}{1 - \frac{\Delta V_a}{V_{DD} - V_{Tn}}}\right)} \\ &= \ln\left(\frac{1}{1 - \frac{\Delta V_{out}}{V_{DD}}} - \frac{1}{1 - \frac{\Delta V_a}{V_{DD} - V_{Tn}}}\right) \end{aligned} \quad (1)$$

For $\Delta V_{out} = 0.6V$, $\Delta V_a = 1.4V$, thus $\frac{C_a}{C_L} =$.

For $\Delta V_{out} = 0.8V$, $\Delta V_a = 1.2V$, thus $\frac{C_a}{C_L} =$.

Thus, $\leq \frac{C_a}{C_L} \leq$.

b

For (i) A = 0, B = 0 to 1:

C_a is charged in precharge phase. Thus both C_L and C_a need to be discharged in evaluation phase.

For (ii) B = 1, A = 0 to 1:

Only C_L is charged in precharge phase. Thus only C_L needs to be discharged in evaluation phase.

Thus, case (ii) results in the lower high-to-low delay.