

Typically, the clock edges arrive together for Reg. A & B.
That is, $t_{clk,A} = t_{clk,B}$

Clock Frequency :-

$$t_{clk} = \underbrace{t_{c-q}(A)}_{\text{For "A"}} + t_{logic-max} + \underbrace{t_{su}(B)}_{\text{For "B"}}$$

The data arriving at Reg. A will be available after $t_{c-q}(A)$ at the logic block. The logic block will produce a delay of $t_{logic-max}$. And this data must be available $t_{su}(B)$ before the clock arrives at Reg. B.

Hold time :-

The hold time req. for Reg. B indicates that the input to Reg. B should NOT change for at least $t_h(B)$ time units after the clock edge. The soonest the data can arrive at the input of Reg. B is $t_{c-q}(A)_{-min} + t_{logic-min}$.

$$t_{hold}(B) \leq t_{c-q}(A)_{-min} + t_{logic-min}$$

Unfortunately, there are uncertainties in the clock arrival times.

We categorize these into :- $\begin{matrix} \text{SK} \text{E} \text{W} & \rightarrow & \text{spatial} \\ \text{J} \text{I} \text{T} \text{T} \text{E} \text{R} & \rightarrow & \text{temporal} \end{matrix}$


Clock skew is the spatial variation in temporally-equivalent clock edges. Clock skew depends on the routing direction. It is caused by static mismatches in the clock paths and differences in the clock load.

Clock skew \rightarrow Positive
 \rightarrow Negative

Positive clock skew :- Receiving edge arrives later than the launching edge

Negative clock skew :- Receiving edge arrives earlier than the launching edge.

 The definitions of receiving & launching clock edge are with respect to the direction of data flow.



Positive skew analysis :

$$T_{clk} + \underset{\substack{\uparrow \\ \text{skew}}}{\delta} \geq t_{c-q} + t_{setup} + t_{logic-max}$$

$$T_{clk} \geq t_{c-q} + t_{setup} + t_{logic-max} - \delta$$

Possibility to operate the circuit faster

However because of positive skew, there is a likelihood of hold violation!

$$\delta + t_h \leq t_{c-q}(min) + t_{logic-min}$$

$$t_h \leq t_{c-q}(min) + t_{logic-min} - \delta \rightarrow \text{stringent constraint on hold.}$$

Worst case for race condition is when the receiving edge of the clock arrives late.

Negative skew analysis :

$$T_{clk} - \delta \geq t_{c-q} + t_{logic} + t_{su}$$

$$T_{clk} \geq t_{c-q} + t_{logic} + t_{su} + \delta$$

Clock Frequency reduces with Negative skew.

In this case no race condition is ever possible.

Summary of clock skew :-

- +ive :- improves performance + degrades reliability
- ive :- degrades performance + improves reliability.

Remember :- Worst case performance when receiving clock edge arrives early.

... race condition when receiving clock

⇒ due to skew.

Remember

arrives early.

Worst case race condition when receiving clock edge arrives late.

⇒ due to skew

Clock Jitter :

Jitter is the temporal variation in the arrival of clock edge at a given location on the chip. This leads to a change in the clock period.

Worst case performance due to both skew & jitter will be given as :-

$$T_{clk} \geq t_{c-q} + t_{logic} + t_{su} + \delta + 2t_{jitter}$$

Receiving edge arrives early & launching edge arrives late

Worst case for race condition due to skew & jitter :-

$$t_{hold} \leq t_{c-q \min} + t_{logic \min} - \delta - 2t_{jitter}$$

launching edge arrives early & receiving edge arrives late

Performance worst case :-

Receiving edge early & launching edge late

Reliability or race condition worst case :-

Receiving edge late & launching edge early

⇒ Both jitter & skew